

COMP311-5: Logic Circuit Design

Spring 2019, Prof. Taigon Song

Quiz #1: March 26, 9:00 – 10:00am [Total: 105 points]

1. Design an inverter that has the module name of "inverter".

You must have an "assign" statement inside your design. [10 points]

2. Describe the period of clk1 and clk2 in nanoseconds (ns). [10 points each, 20 total]

```
`timescale 1ns / 1ns

module XORgate_tb();
  wire out1234567890;
  reg clock1, clock2;

  always begin
    #2 clock1 = ~clock1;
  end

  always begin
    #4 clock2 = ~clock2;
  end

  initial begin
    clock1 = 0;
    clock2 = 0;
  end

  XORgate tgxor1(clock1, clock2, out1234567890);
endmodule
```


3. Convert '13' (decimal) to binary, then express this in Verilog. [20 points total]

(1) how many bits do you need? [10 points]

(2) use the Verilog expression to represent 13. [10 points]

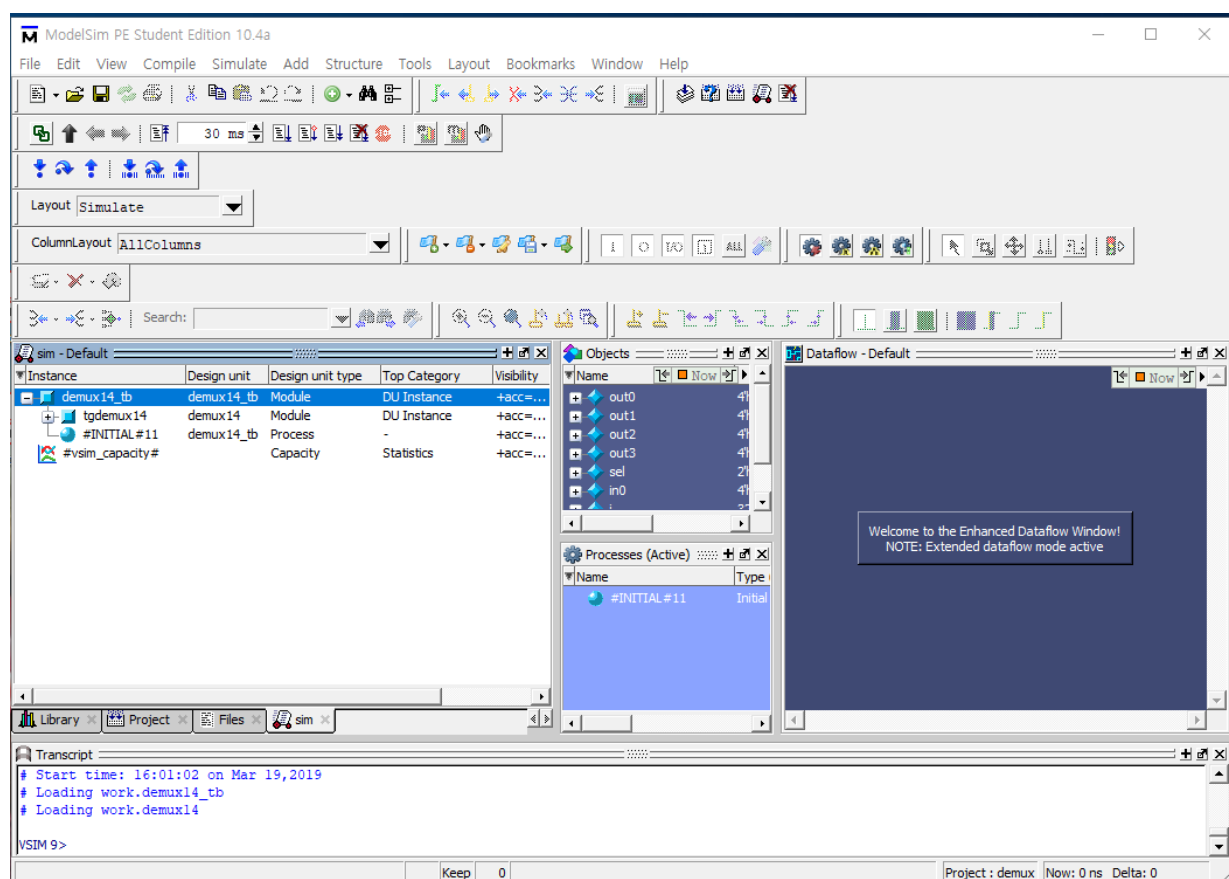4. Please describe the next step to be performed based on the Modelsim tutorial. [10 points]

(Hint, I finished compile, then ran "simulate" in Library→work→demux14_tb)




5. Please design a 2:1 mux using the following design methodologies.

Below will be a common syntax this problem. If you need additional statements to detail your methodology, you are welcome to describe them.

[3 points each]

```
module mux21(output y, input i0, i1, s);  
  (fill in here)  
endmodule
```

(1) Using primitive gates

 

(2) Using primitive gates, but not using INV

(3) Using only one AND keyword

(4) using the "assign" statement, no ternary operator

(hint, $Y = I0 \circ S' + I1 \circ S$)

(5) using the "assign" statement, with ternary operator

(6) Using "if/else" statement

(Hint: you may need something more for (6) and (7)).

(7) Using "case" statement

5. Find the inappropriate statements in the following designs. You are to design an optimized 1:4 demultiplexer.

[12 errors in total, 2 points each]

<pre> module demux14(in0, sel, out0, out1, out2, out3) input [3:0] in0; input [2:0] sel; output reg [3:0] out0, out1, out2, out3; wire select; always @(!) begin case(sel) 2'b11 : begin out0 <= in0; out1 <= 4'b0000; out2 <= 4'b0000; out3 <= 4'b0000; end 2'b01 : begin out0 <= 4'b0000; out1 <= in0; out2 <= 4'b0000; out3 <= 4'b0000; end 2'b11 : begin out0 <= 4'b0000; out1 <= 4'b0000; out2 <= in0; out3 <= 4'b0000; end default : begin out0 <= 4'b0000; out1 <= 4'b0000; out2 <= 4'b0000; out3 <= in0; end endcase end endmodule </pre>	<pre> `timescale 1ns / 10ns module demux14_tb(inout leon); wire [3:0] out0, out1, out2, out3, out4; reg [1:0] sel; reg [3:0] in0; wire i; demux14 tgdemux14(.in0(in10), .sel(sel), .out0(out0), .out1(out1), .out2(out2), .out3(out3)); initial begin in0 <= \$random; sel <= 0; for(i=1; i <4; i++) #10000 sel <= i; end endmodule </pre>
---	--