



COMP311-1 Logic Circuit Design


Chap. 2

Instructor: Taigon Song (송대건)

2019 Fall

Modelsim Tutorial [1/10]

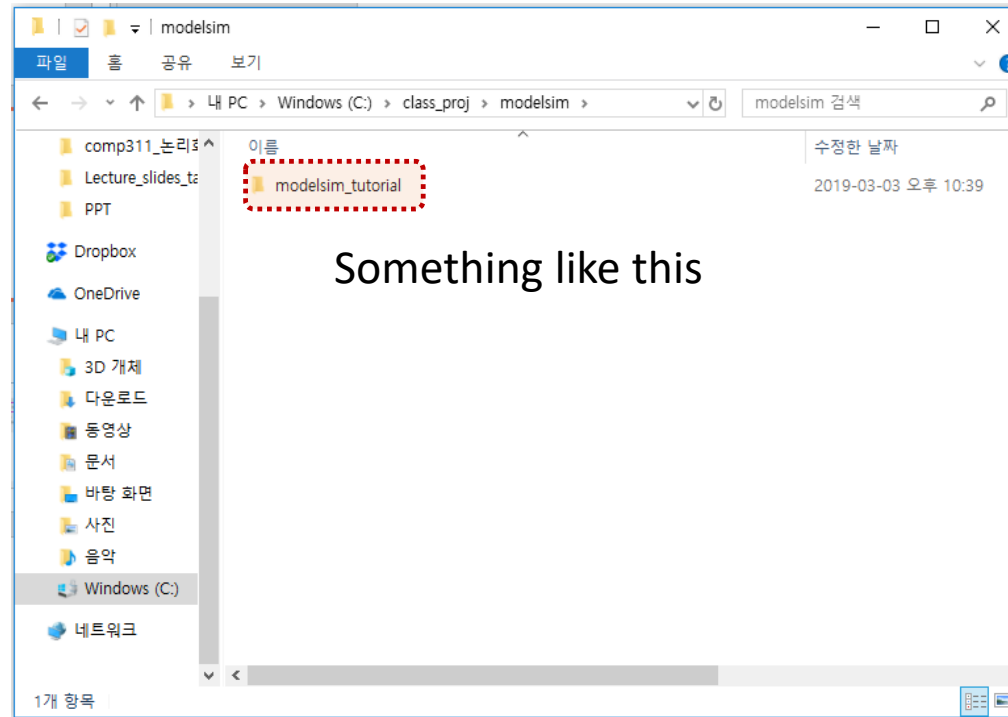- Create a folder in the location you desire




- Note)
 - Always in (D:) when using the lab desktop
 - No Korean
 - No spaces

Modelsim Tutorial [2/10]


- Copy two files from the Modelsim installation directory
 - counter.v and tcounter.v

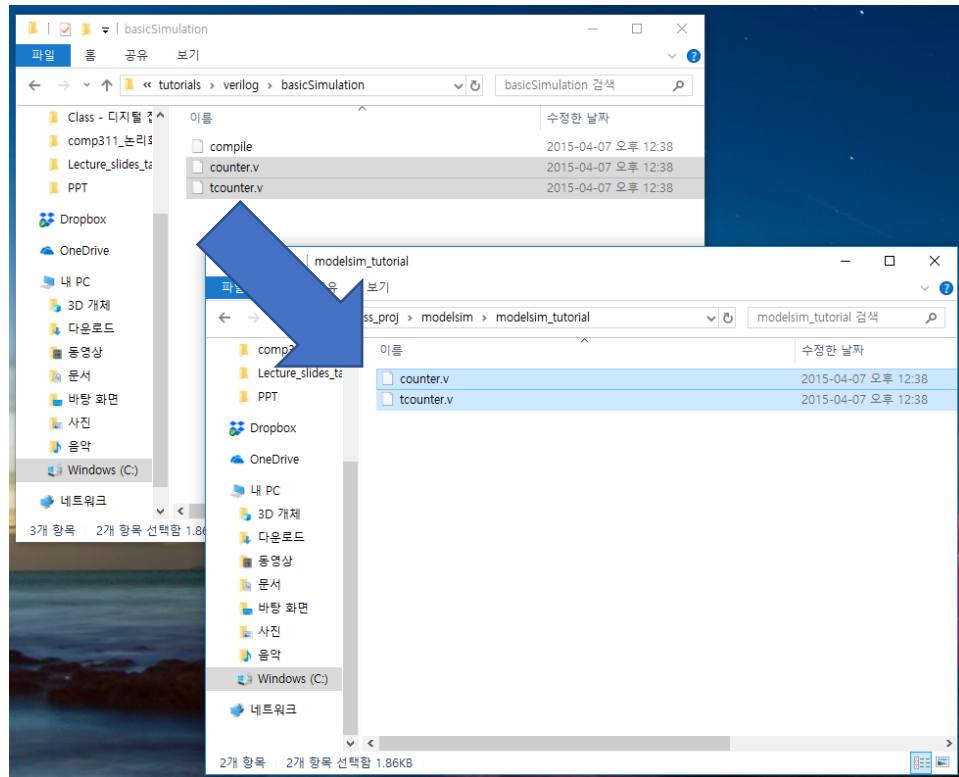Verilog – `<install_dir>/examples/tutorials/verilog/basicSimulation/counter.v` and `tcounter.v`




Modelsim Tutorial [3/10]

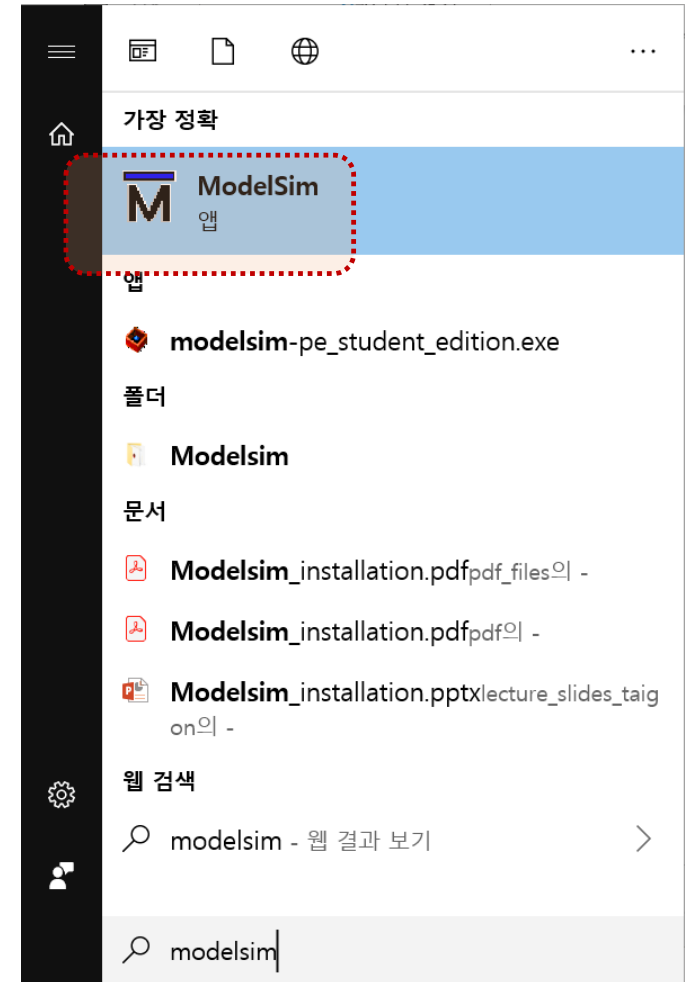- Run modelsim
 - Run in administrative mode when you're having problems executing in default permission settings




Modelsim Tutorial [4/10]

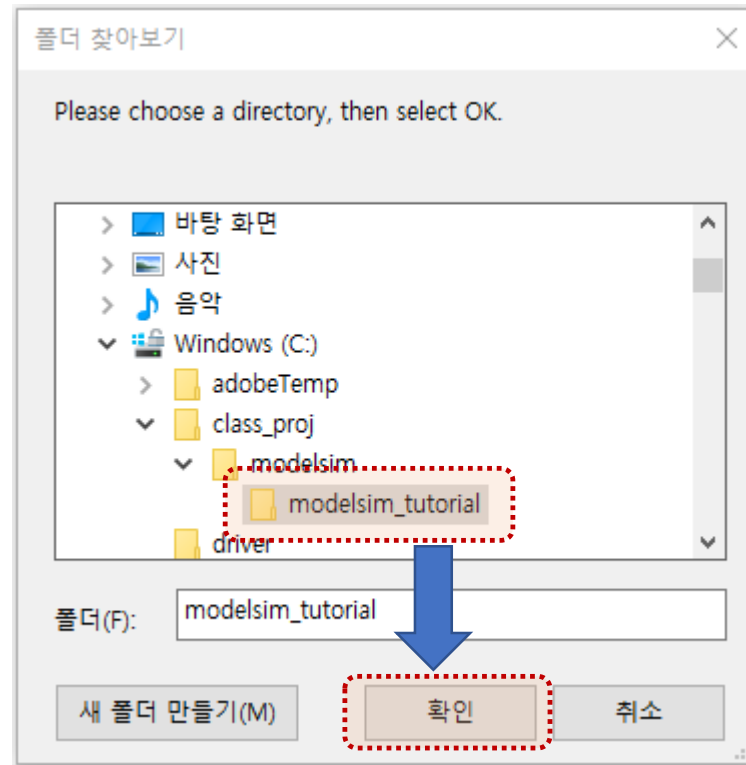- File → Change directory
 - Change it to the directory that you created and copied the two Verilog files. (counter.v and tcounter.v)
- Then OK







Modelsim Tutorial [5/10]

 - File → New → Project
 - Change the Project Name, and don't change any other items
- Then OK






Modelsim Tutorial [6/10]

 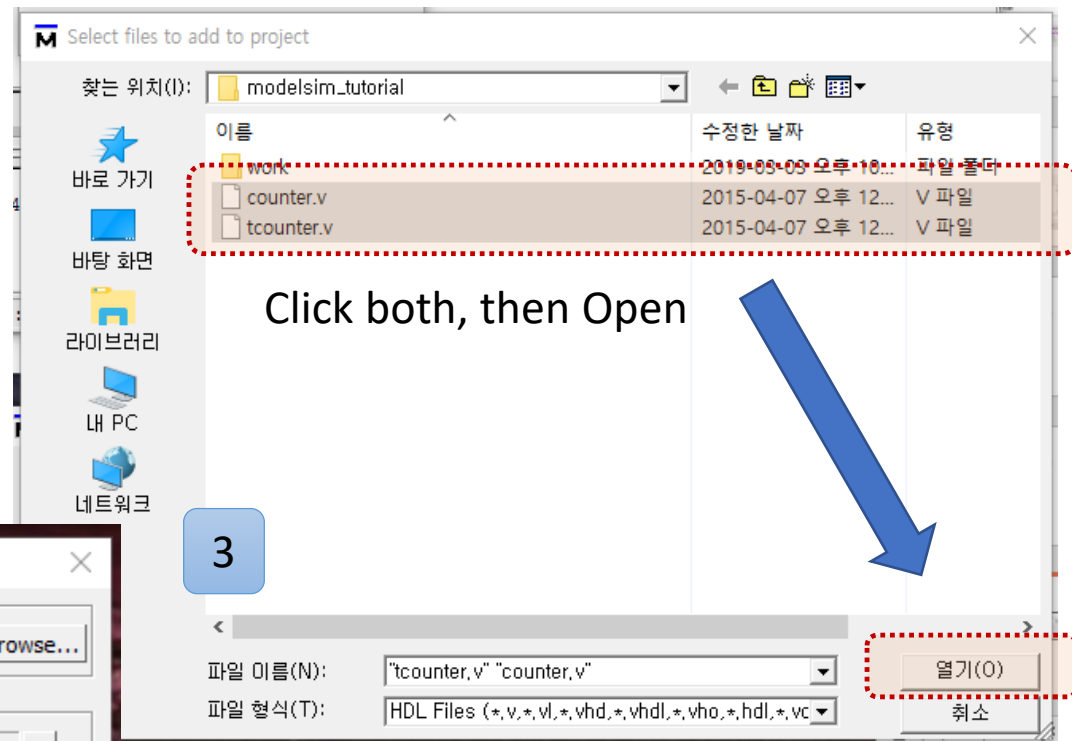 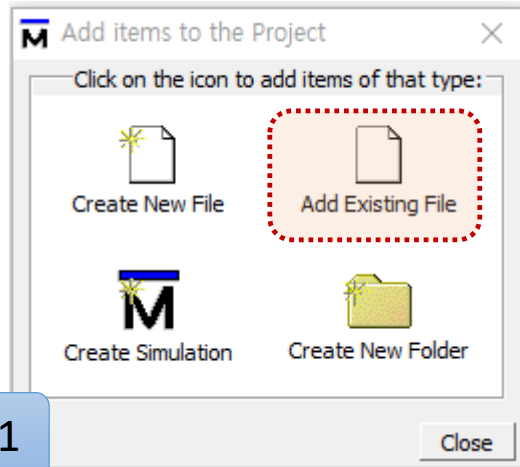



Modelsim Tutorial [7/10]

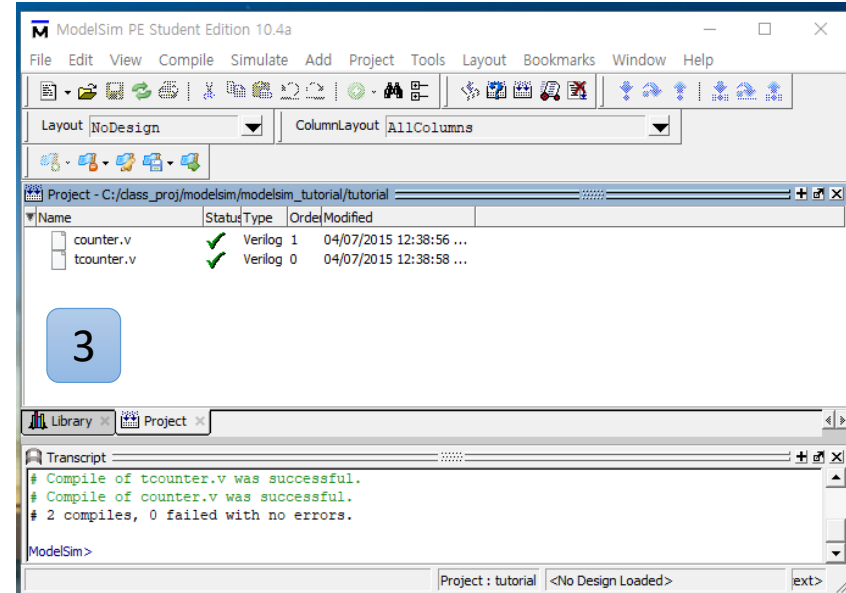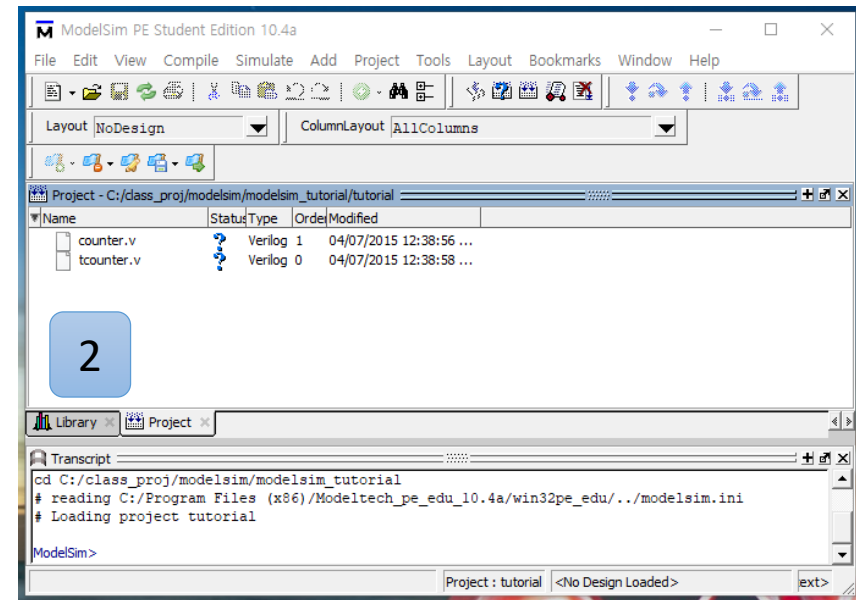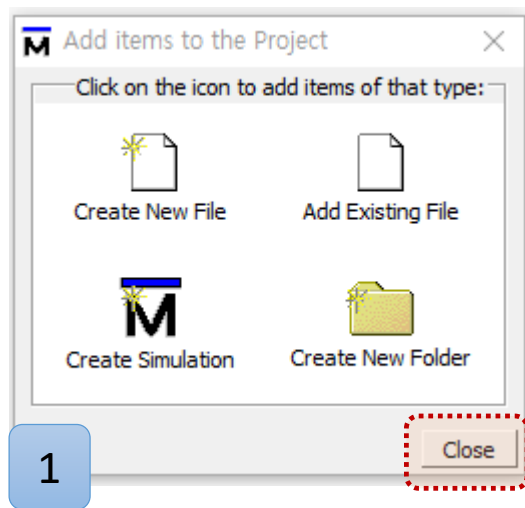- Close “Add items to the Project”
- Compile → Compile all
 - Make sure “?” changes to “√”



Modelsim Tutorial [8/10]

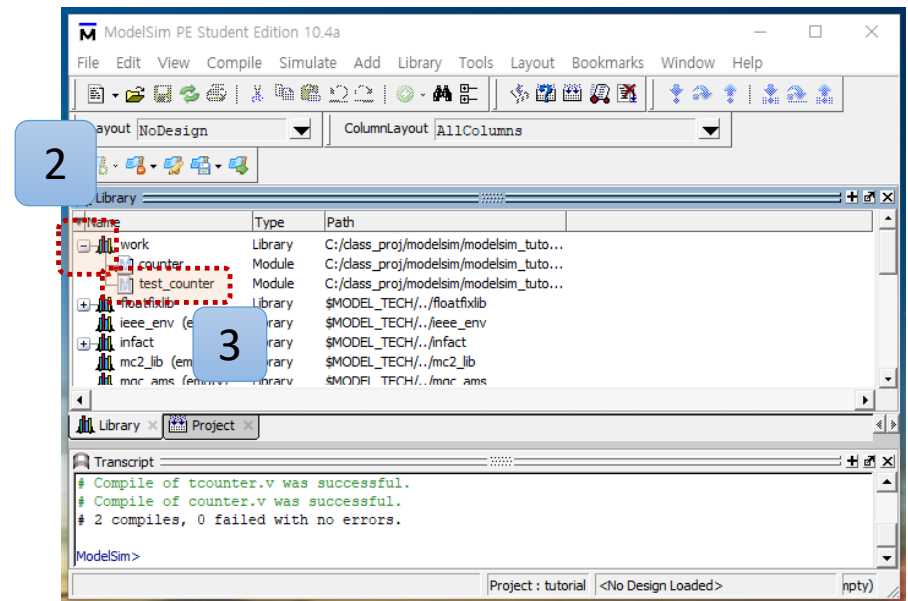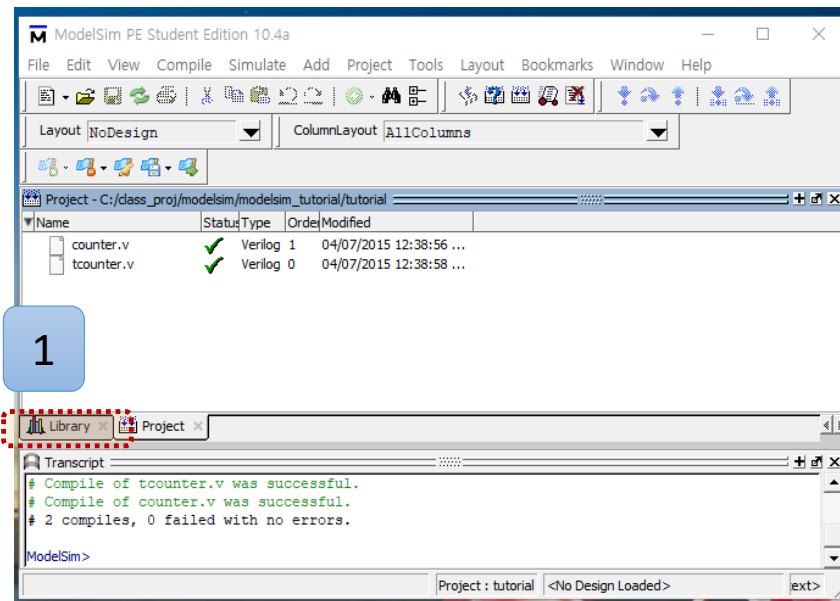
- Click “Library tab”, then click the “+” icon next to the “work”



- Then, right click “test_counter” → simulate

Modelsim Tutorial [9/10]

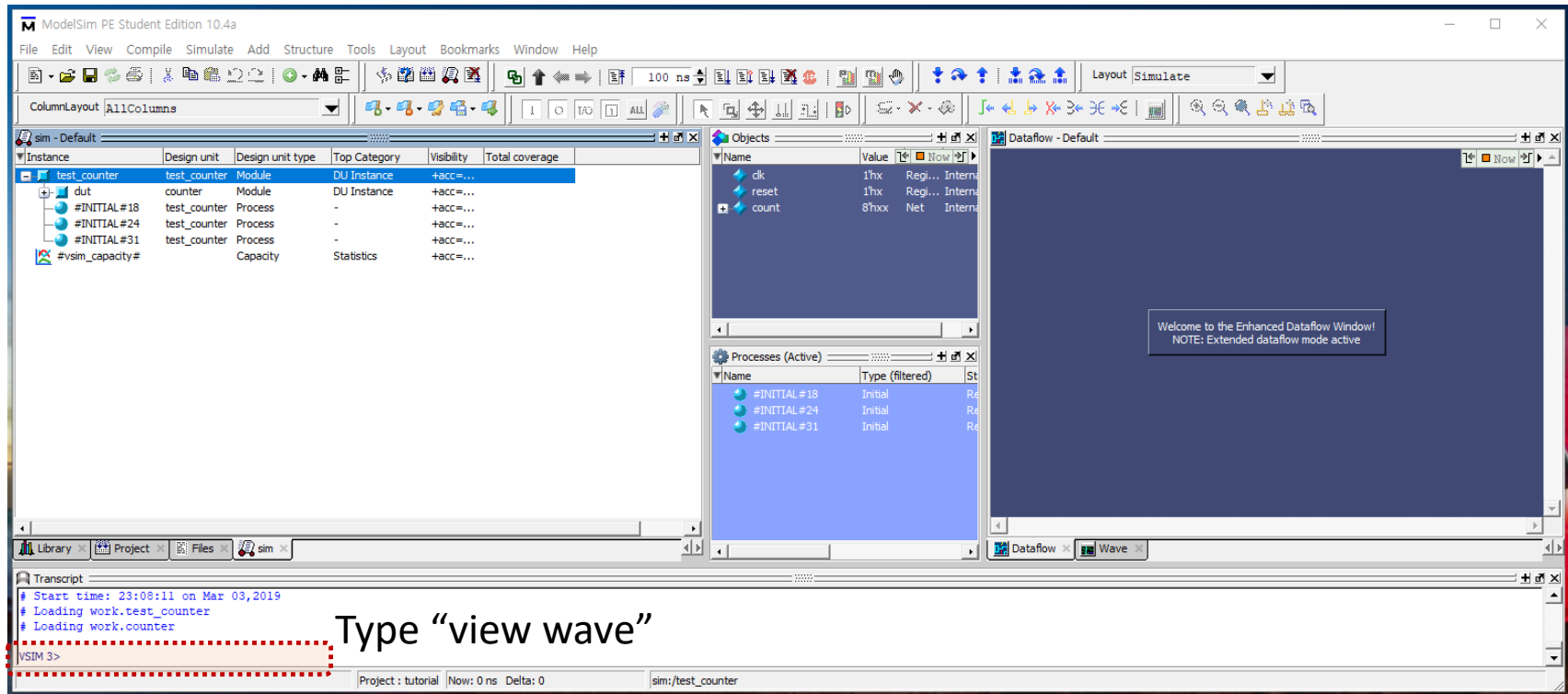
- After (9), you will see something like this:




- Type “view wave” in the command prompt.
- Then, Add → To Wave → All items in Region

Modelsim Tutorial [10/10]

- Click the “Run” icon

 


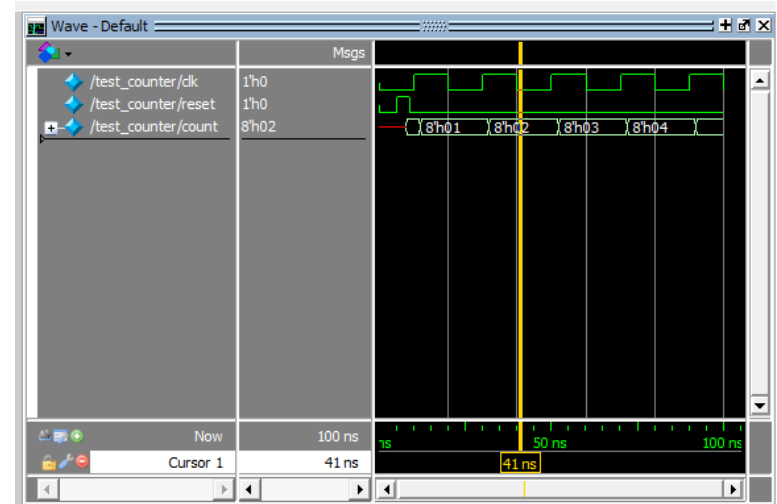- In the wave view, right click → zoom full
- Then, you'll see something like this




Design Methodologies

- Top-down


 


- Bottom-up

 


A 4-bit Ripple Carry Counter Example

 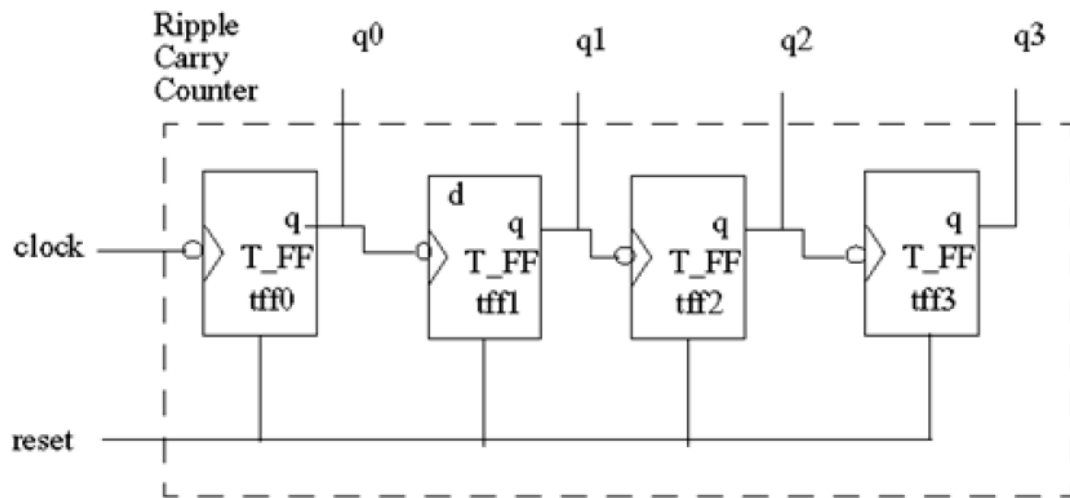- Based on negative edge-triggered toggle flipflops (T_FF)



Design Hierarchy

Example of the “Ripple Carry Counter”

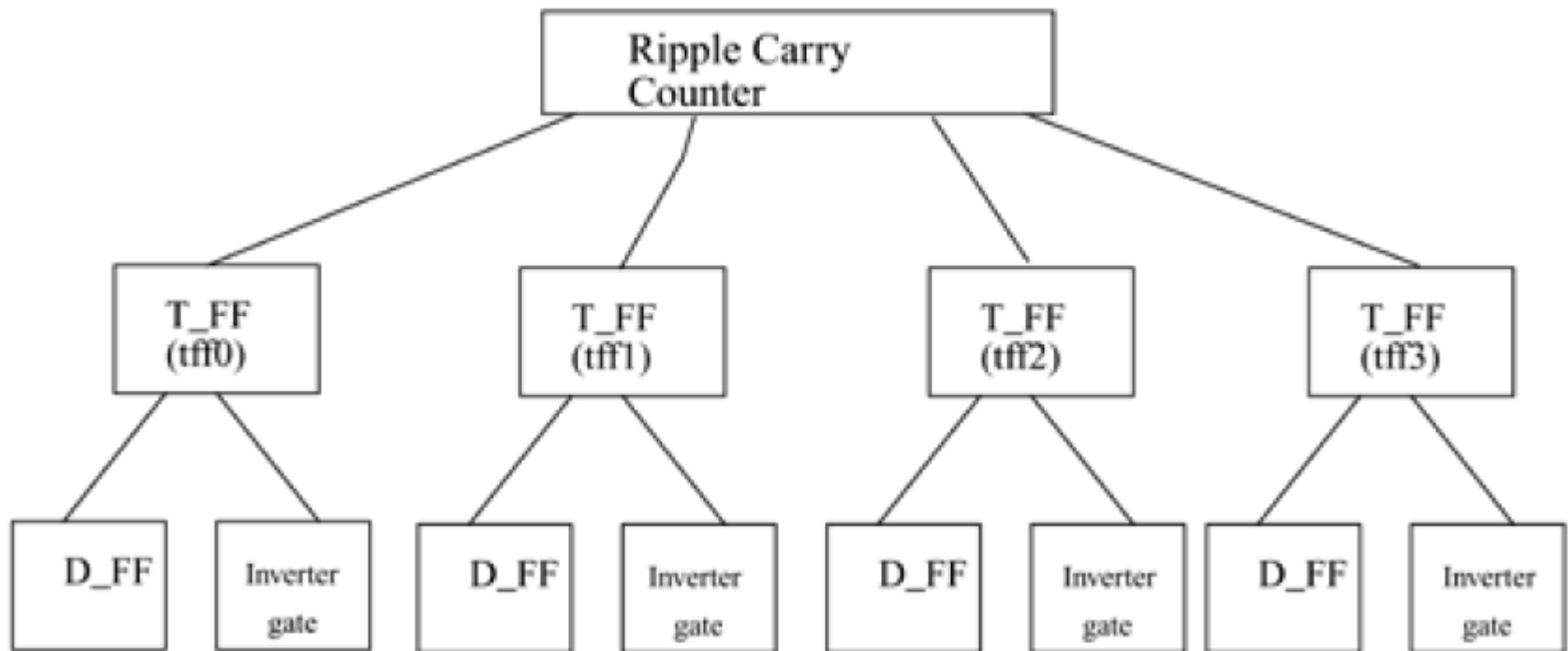

Syntax of a Module Definition

```
module <module_name>
  (<module_terminal_list>);
  ...
  <module internals>
  ...
  ...
endmodule
```

```
module T_FF (q, clock, reset);
  .
  .
  <functionality of T-flipflop>
  .
  .
endmodule
```

Levels of Design Abstraction

- Behavioral or algorithmic level
 - Highest level of abstraction. Almost as similar to C programming
- Dataflow level
 - How data flows between HW registers and how data is processed
- Gate level
 - AND, OR, INV...etc
- Switch level
 - Transistor level

Instances

- A unique object summoned from a module definition

```
// Define the top-level module called ripple carry
// counter. It instantiates 4 T-flipflops. Interconnections are
// shown in Section 2.2, 4-bit Ripple Carry Counter.
module ripple_carry_counter(q, clk, reset);

output [3:0] q; //I/O signals and vector declarations
               //will be explained later.
input clk, reset; //I/O signals will be explained later.

//Four instances of the module T_FF are created. Each has a unique
//name.Each instance is passed a set of signals. Notice, that
//each instance is a copy of the module T_FF.
T_FF tff0(q[0],clk, reset);
T_FF tff1(q[1],q[0], reset);
T_FF tff2(q[2],q[1], reset);
T_FF tff3(q[3],q[2], reset);

endmodule
```

```
// Define the module T_FF. It instantiates a D-flipflop. We assumed
// that module D-flipflop is defined elsewhere in the design. Refer
// to Figure 2-4 for interconnections.
module T_FF(q, clk, reset);

//Declarations to be explained later
output q;
input clk, reset;
wire d;

D_FF dff0(q, d, clk, reset); // Instantiate D_FF. Call it dff0.
not n1(d, q); // not gate is a Verilog primitive. Explained later.

endmodule
```

Illegal Module nesting


- What is the problem here?

```
// Define the top-level module called ripple carry counter.  
// It is illegal to define the module T_FF inside this module.  
module ripple_carry_counter(q, clk, reset);  
output [3:0] q;  
input clk, reset;  
  
    module T_FF(q, clock, reset); // ILLEGAL MODULE NESTING  
    ...  
    <module T_FF internals>  
    ...  
endmodule // END OF ILLEGAL MODULE NESTING  
  
endmodule
```


A Verilog Experiment

Understanding the concept of “testbench”

 - What's the difference between a normal module and a testbench module?



Testbench module

 

Ripple Carry Counter module

A Verilog Experiment

What are needed in a Testbench.v

