



# COMP311-1 Logic Circuit Design


## Chap. 4

Instructor: Taigon Song (송대건)

2019 Fall
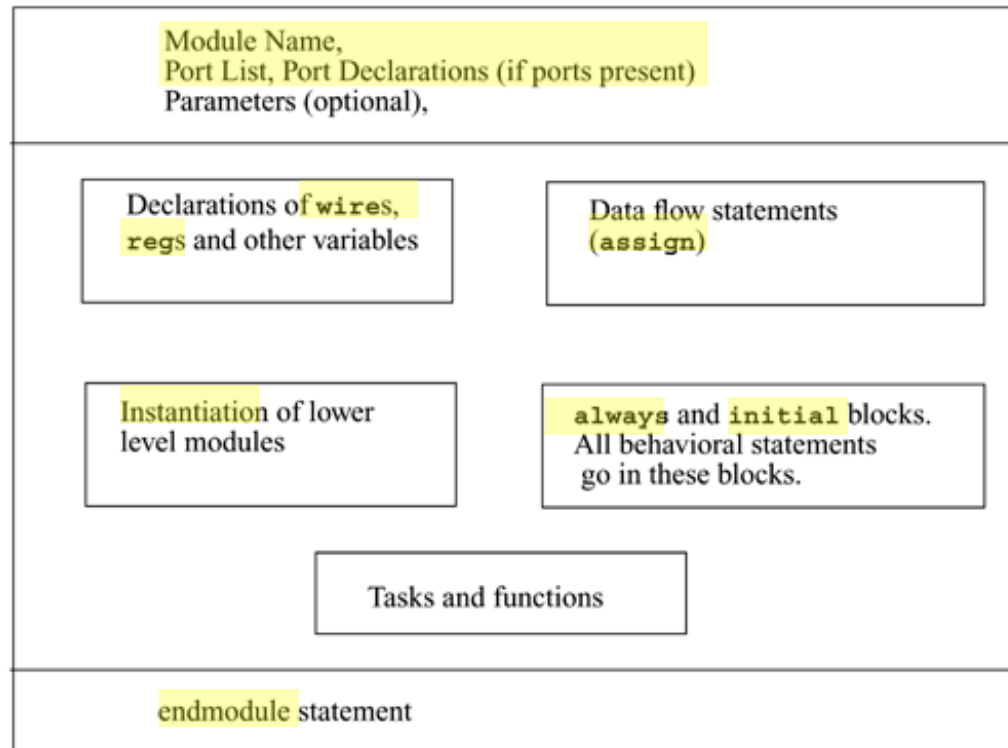
# 4.1. Modules

- Module: The basic building block in Verilog
  - Essential: module, module name, endmodule
  - Note: If no compile error, ordering is not an issue...?



# 4.1. Modules


## *A Latch example*

```
// This example illustrates the different components of a module
// Module name and port list
// SR_latch module
module SR_latch(Q, Qbar, Sbar, Rbar);

//Port declarations
output Q, Qbar;
input Sbar, Rbar;

// Instantiate lower-level modules
// In this case, instantiate Verilog primitive nand gates
// Note, how the wires are connected in a cross-coupled fashion.
nand n1(Q, Sbar, Qbar);
nand n2(Qbar, Rbar, Q);

// endmodule statement
endmodule
```

 

```
// Module name and port list
// Stimulus module
module Top;

// Declarations of wire, reg, and other variables
wire q, qbar;
reg set, reset;

// Instantiate lower-level modules
// In this case, instantiate SR_latch
// Feed inverted set and reset signals to the SR latch
SR_latch m1(q, qbar, ~set, ~reset);


// Behavioral block, initial
initial
begin
    $monitor($time, " set = %b, reset= %b, q= %b\n",set,reset,q);
    set = 0; reset = 0;
    #5 reset = 1;
    #5 reset = 0;
    #5 set = 1;
end

// endmodule statement
endmodule
```

## 4.2. Ports
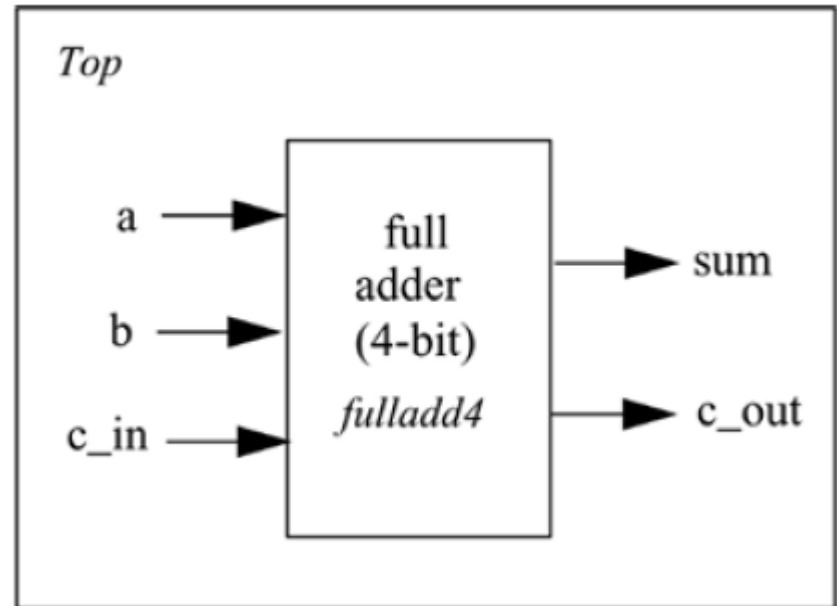
### *List of Ports*

- Ports: Provide the interface by which a module can communicate with its environment
  - Either Input or Output (I/O)
  - “terminals” in other words
- Details of Fig. 4-3.
  - Top: top-level module
  - Input: a, b, c\_in
  - Output: sum, c\_out



```
module fulladd4(sum, c_out, a, b, c_in); //Module with a list of ports
module Top; // No list of ports, top-level module in simulation
```

## 4.2. Ports

### *Port Declaration*

- Input, output, or inout
  - If a port holds value, it should be **reg**
  - Inout cannot be reg

```
module fulladd4(sum, c_out, a, b, c_in);  
  
    //Begin port declarations section  
    output[3:0] sum;  
    output c_out;  
  
    input [3:0] a, b;  
    input c_in;  
    //End port declarations section  
    ...  
<module internals>  
    ...  
endmodule
```

Verilog Keyword	Type of Port
input	Input port
output	Output port
inout	Bidirectional port

```
module DFF(q, d, clk, reset);  
    output q;  
    reg q; // Output port q holds value; therefore it is declared as reg.  
    input d, clk, reset;  
    ...  
    ...  
endmodule
```

## 4.2. Ports

### *Port Declaration*

- Can be declared like this too
  - ANSI C style


```
module fulladd4(output reg [3:0] sum,
               output reg c_out,
               input [3:0] a, b, //wire by default
               input c_in); //wire by default
...
<module internals>
...
endmodule
```

## 4.2. Ports

### *Port Connection Rules*

- Connection rules must be followed
  - Inputs: internally, input ports are always 'net' type
  - Outputs: internally, output ports can be 'reg' or 'net' type
  - Inouts: internally, inout ports must always be 'net' type
  - Width matching: internal and external port widths should match
    - Warning when not matched

**Figure 4-4. Port Connection Rules**

 

## 4.2. Ports

### *Port Connection Rules*

- Unconnected ports
  - Ports can be unconnected for certain reasons

```
fulladd4 fa0(SUM, , A, B, C_IN); // Output port c_out is unconnected
```

- Illegal situations
  - Internal output connected to a reg

#### **Example 4-3 Port Declarations**

```
module fulladd4(sum, c_out, a, b, c_in);  
  
    //Begin port declarations section  
    output[3:0] sum;  
    output c_out;  
  
    input [3:0] a, b;  
    input c_in;  
    //End port declarations section  
    ...  
<module internals>  
    ...  
endmodule
```

#### **Example 4-6 Illegal Port Connection**

```
module Top;  
  
    //Declare connection variables  
    reg [3:0] A,B;  
    reg C_IN;  
    reg [3:0] SUM;  
    wire C_OUT;  
  
    //Instantiate fulladd4, call it fa0  
    fulladd4 fa0(SUM, C_OUT, A, B, C_IN);  
    //Illegal connection because output port sum in module fulladd4  
    //is connected to a register variable SUM in module Top.  
    .  
    .  
<stimulus>  
    .  
    .  
endmodule
```



## 4.2. Ports

### *Connecting Ports to External Signals*

- Two methods possible, cannot be mixed
- Connecting by ordered list
  - Same order as the ports in the module definition

#### Example 4-7 Connection by Ordered List

```
module Top;

//Declare connection variables
reg [3:0]A,B;
reg C_IN;
wire [3:0] SUM;
wire C_OUT;

    //Instantiate fulladd4, call it fa_ordered.
    //Signals are connected to ports in order (by position)
    fulladd4 fa_ordered(SUM, C_OUT, A, B, C_IN);
    ...
    <stimulus>
    ...
endmodule
```

```
module fulladd4(sum, c_out, a, b, c_in);
output[3:0] sum;
output c_out;
input [3:0] a, b;
input c_in;
    ...
    <module internals>
    ...
endmodule
```

- Connecting by name
  - Port name can be rearranged, ports can be dropped

```
// Instantiate module fa_byname and connect signals to ports by name
fulladd4 fa_byname(.c_out(C_OUT), .sum(SUM), .b(B), .c_in(C_IN),
    .a(A), );
```

```
(.sum(SUM), .b(B), .c_in(C_IN), .a(A), );
```


## 4.3. Hierarchical Names

- Every module instance, signal, or variable is defined with an identifier
  - A particular identifier has a unique place in the design hierarchy
  - A hierarchical name is a list of identifiers separated by 'dots' for each level of hierarchy
  - %m when printing in \$display

- E.g.) at any module:

```
initial $display("Hierarchy of this module: %m");
```

Figure 4-5. Design Hierarchy for SR Latch Simulation

 

### Example 4-8 Hierarchical Names


```
stimulus
stimulus.qbar
stimulus.reset
stimulus.m1.Q
stimulus.m1.S
stimulus.n1
```

```
stimulus.q
stimulus.set
stimulus.m1
stimulus.m1.Qbar
stimulus.m1.R
stimulus.n2
```

# In class assignment
 
## *Design a 2:1 MUX*

- $Y = I0 \circ S' + I1 \circ S$
- By
  1. Primitive gates (1)
  2. (2) – not using INVs
  3. (3) – using only one AND keyword in the .v file
  4. Using the “assign” statement (1)
  5. (2) – using ternary operator (a ? b : c)
  6. Using “if/else” statement
  7. Using “case” statement





S	I1	I0	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

# In class assignment
  
## *Design a 2:1 MUX*

- Primitive gates
  - not (out, in1)
  - buf (out, in1)
  - and (out, in1, in2, ..., inN)
  - or (out, in1, in2, ..., inN)
  - nand (out, in1, in2, ..., inN)
  - nor (out, in1, in2, ..., inN)
  - xor (out, in1, in2, ..., inN)
  - xnor (out, in1, in2, ..., inN)



# In class assignment

## *Design a 2:1 MUX*

- If (inside initial/always)

```
if (condition-1)
    statement-1;
else if(condition-2)
    statement-2;
...
else
    statement N
```

- Case (inside initial/always)

```
case (ctrl_sig)
    value-1: statement1;
    value-2: statement1;
    value-3: statement1;
    ...
    default: statementN;
endcase
```

# Homework #2

## *Design a 4:1 mux*

- Design a 4:1 mux
  - 4bit input
  - 4bit output
  - Use \$random when assigning initial values for your input
  - Use 'for' statement to change your sel values
  - Use any design methodology you prefer
- Due: 9/23 8:59am
  - Explain in simple words how you designed your module and testbench.
  - Screen capture your waveform results.
  - Write down both your .v and \_tb.v in your report
  - Homework report should not exceed 3 pages. No cover page required. Report required to be submitted in English.
  - 3 pages, PDF online, and paper offline.